



Cyprus  
University of  
Technology

## EEN442 - Power Systems II (Συστήματα Ισχύος II)

Part 2: Fundamentals of power system operation

<https://sps.cut.ac.cy/courses/een442/>

Dr Petros Aristidou

Department of Electrical Engineering, Computer Engineering & Informatics

Last updated: September 4, 2023


After this part of the lecture and additional reading, you should be able to . . .

- 1 . . . describe and analyse the behaviour of a transmission line under different operating conditions;
- 2 . . . explain the Ferranti effect;
- 3 . . . use the  $PV$  and  $P - \delta$  characteristics to determine the steady-state voltage and angle stability of a power system.

- In this part of the lecture, we investigate the stationary current and voltage relations as well as the resulting active and reactive power flows on an AC power line
- For this purpose, we use the wave equation discussed in EEN320
- Thereby, we focus on a series of practically relevant scenarios
- The analysis is performed under two assumptions:
  - 1) The operating conditions are balanced → analysis is performed via single-phase equivalent circuits
  - 2) The network is in steady-state (for assessment of dynamic phenomena other models are required)
- Furthermore, we consider all powers *per phase*. The corresponding three-phase power can be calculated using the conventions introduced in Part 1.

- 1 **Decoupled quantities**
- 2 **Surge impedance loading**
  - Surge impedance loading of a lossless power line
  - Surge impedance loading of a lossy power line
- 3 **The two extrema: No load and short circuit conditions**
  - No load conditions
  - Short circuit conditions
- 4 **Reactive power demand of a power line**
- 5 **Voltage drop across a power line**
- 6 **Efficiency of a high-voltage power line**
- 7 **Voltage-active power (P-V) characteristic of a high-voltage power line**
- 8 **Angle-active power (P- $\delta$ ) characteristic of a high-voltage power line**

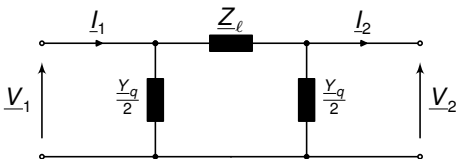- 1 **Decoupled quantities**
- 2 Surge impedance loading
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power ( $P-V$ ) characteristic of a high-voltage power line
- 8 Angle-active power ( $P-\delta$ ) characteristic of a high-voltage power line



where:


$$\underline{Z}_\ell = \underline{Z}_W \sinh(\underline{\gamma}\ell)$$

$$\frac{Y_q}{2} = \frac{\cosh(\underline{\gamma}\ell) - 1}{\underline{Z}_W \sinh(\underline{\gamma}\ell)} = \frac{1}{\underline{Z}_W} \tanh\left(\frac{\underline{\gamma}\ell}{2}\right)$$

$$\underline{\gamma} = \sqrt{(R' + j\omega L')(G' + j\omega C')}$$

$$\underline{Z}_W = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

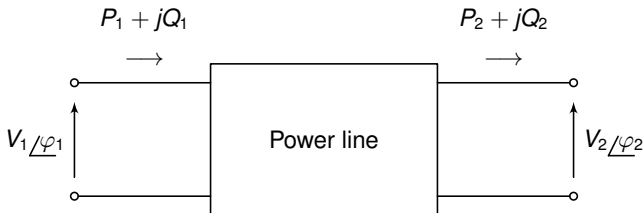These parameters correspond to exact relations between currents and voltages according to wave equation for  $x = 0$  and  $x = \ell$




- Several ways to mathematically describe power flow over a power line
- Usually, we use complex voltage together with active and reactive powers at each end of line
- This yields 8 real quantities

$$V_1, \varphi_1, P_1, Q_1, V_2, \varphi_2, P_2, Q_2$$


- Which of the above quantities are decoupled (i.e. independent) of each other and which are not?

# 1 Decoupled quantities - Examples

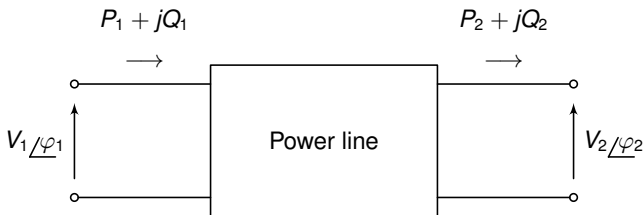


- Not all quantities in above graphic are independent of each other
- Examples:
  - $\underline{V}_1$  and  $\underline{V}_2$  are coupled via line characteristics (see previous lectures)
  - Therefore it is customary to take one angle, e.g.  $\varphi_2$ , as reference; hence, one "loses" one quantity in the formulas
  - Power flows are also coupled; if  $P_1$  and  $Q_1$  are fixed, then  $P_2$  and  $Q_2$  can be computed if  $\underline{V}_1$  or  $\underline{V}_2$  is fixed, too
  - If  $\underline{V}_1$  and  $\underline{V}_2$  are fixed,  $P_1$ ,  $P_2$ ,  $Q_1$  and  $Q_2$  are also fixed and can *not* be adjusted independently



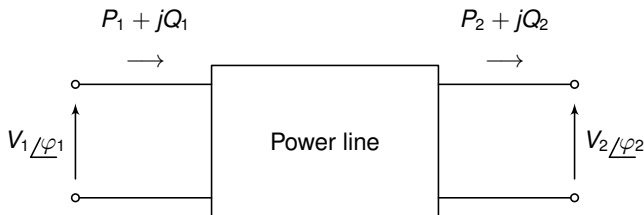

- $V_1, \varphi_1, V_2$ : powers result from line characteristics and given quantities; practical example: power line connects two bulk "stiff" power networks
- $V_1, P_2, Q_2$  (or  $P_1, Q_1, V_2$ ): By fixing voltage on one end of line and power on other end, remaining quantities follow; practical example: consumer with fixed power demand connected via power line to network
- $V_1, P_1, Q_1$ : By fixing quantities at sending end of line, voltage and powers at receiving end follow; practical example: power plant that feeds network over power line


- 1 Decoupled quantities
- 2 **Surge impedance loading**
  - Surge impedance loading of a lossless power line
  - Surge impedance loading of a lossy power line
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power ( $P$ - $V$ ) characteristic of a high-voltage power line
- 8 Angle-active power ( $P$ - $\delta$ ) characteristic of a high-voltage power line

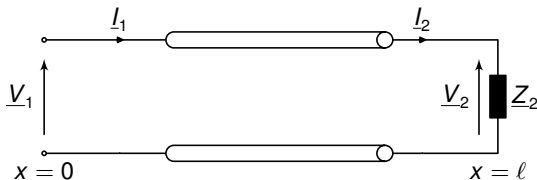

- Surge impedance loading (SIL) = power delivered when line is loaded with its surge impedance, i.e.

$$\underline{Z}_2 = \underline{Z}_w = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

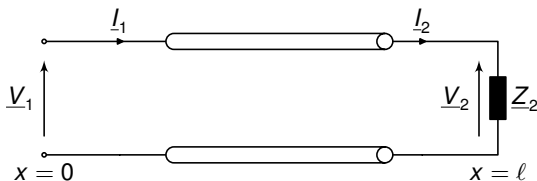- SIL also called natural loading
- In the following, we consider two cases
  - Lossless line ( $R' = G' = 0$ )
  - Lossy line ( $R' \neq 0, G' \neq 0$ )



- Lossless power line:  $R' = G' = 0 \rightarrow$  surge impedance  $Z_w = \sqrt{\frac{L'}{C'}}$

- Active power delivered at end of line


$$P_2 = \frac{|V_2|^2}{Z_2} = \frac{|V_2|^2}{Z_w}$$

- Reactive power delivered at end of line ( $Z_2 = Z_w$  is real in lossless case)

$$Q_2 = 0$$

- Current at end of line
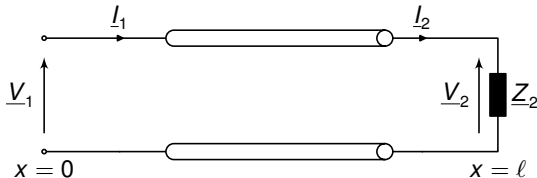
$$I_2 = \frac{V_2}{Z_2} = \frac{V_2}{Z_w}$$



- From full line model equations with  $x = 0$  and  $\underline{\gamma} = j\omega\sqrt{L'C'} = j\beta$


$$\underline{V}_1 = \cosh(j\beta l)\underline{V}_2 + \underline{Z}_W \sinh(j\beta l)\underline{I}_2$$

$$\underline{I}_1 = \frac{\underline{V}_2}{\underline{Z}_W} \sinh(j\beta l) + \cosh(j\beta l)\underline{I}_2$$

- With  $\cosh(j\beta) = \cos(\beta)$  and  $\sinh(j\beta) = j\sin(\beta)$  we obtain

$$\underline{V}_1 = \cos(\beta l)\underline{V}_2 + j\underline{Z}_W \sin(\beta l)\underline{I}_2$$

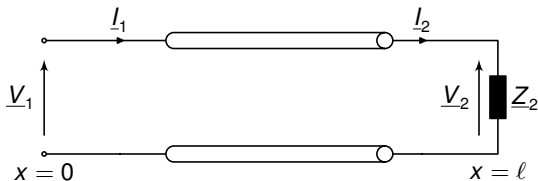
$$\underline{I}_1 = j\frac{\underline{V}_2}{\underline{Z}_W} \sin(\beta l) + \cos(\beta l)\underline{I}_2$$



- Using  $\underline{I}_2 = \frac{\underline{V}_2}{\underline{Z}_2}$  yields

$$\begin{aligned}\underline{V}_1 &= \cos(\beta l)\underline{V}_2 + j\underline{Z}_W \sin(\beta l)\frac{\underline{V}_2}{\underline{Z}_W} \\ &= \underline{V}_2(\cos(\beta l) + j \sin(\beta l)) = \underline{V}_2 e^{j\beta l} \\ \underline{I}_1 &= j\frac{\underline{V}_2}{\underline{Z}_W} \sin(\beta l) + \cos(\beta l)\frac{\underline{V}_2}{\underline{Z}_W} \\ &= \underline{I}_2(\cos(\beta l) + j \sin(\beta l)) = \underline{I}_2 e^{j\beta l}\end{aligned}$$

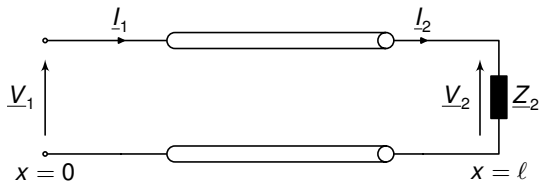→ Voltage and current are shifted by angle  $\beta l$  at end of line  
Thereby, their amplitudes remain unchanged




- For active power at both end of lines, we have that (as line is lossless)

$$P_1 = \underline{V}_1 I_1^* = \underline{V}_2 I_2^* = P_2 = \frac{|\underline{V}_1|^2}{Z_w}$$

- This particular loading of line is called *surge impedance loading (SIL)*

$$P_{SIL} = \frac{|\underline{V}|^2}{Z_w}$$

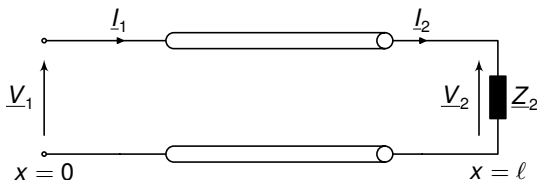- For this loading we achieve optimal transmission conditions (amplitudes of voltage and current remain constant along whole line)
- In practice, loading usually differs from SIL



- For SIL, *reactive power flow on line is zero*
- At each point on line, reactive power "absorption" of line inductance *equals* reactive power "production" of line capacitance


$$Q'_C = Q'_L \Rightarrow V^2 \omega C' = I^2 \omega L' \Rightarrow \frac{V^2}{I^2} = \frac{L'}{C'} = Z_w^2$$



- Surge impedance of overhead lines (OHLs) between 200 – 400  $\Omega$
- OHL inductance significantly larger than OHL capacitance
- Reactive power "absorbed" by OHL inductance exceeds reactive power "produced" by OHL capacitance even for small currents
- OHLs often operated above their SIL; then they "absorb" reactive power
- Compared to OHLs, cables have very low surge impedance ( $\approx 30 - 50 \Omega$ )
- SIL usually above thermal limit of cable
- Cables usually "produce" reactive power

$$P_{SIL} = 50 \text{ MW}$$

$$P_{max} = 100 \text{ MW}$$

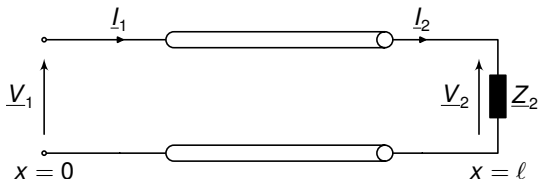


- Lossy line  $\rightarrow \underline{Z}_w$  is complex
- As before, we consider the case  $\underline{Z}_2 = \underline{Z}_w$
- Current at receiving end of line

$$I_2 = \frac{V_2}{\underline{Z}_2} = \frac{V_2}{\underline{Z}_w}$$

- Apparent power at receiving end of line

$$\underline{S}_2 = P_2 + jQ_2 = \underline{V}_2 I_2^* = \frac{|\underline{V}_2|^2}{\underline{Z}_w^*}$$
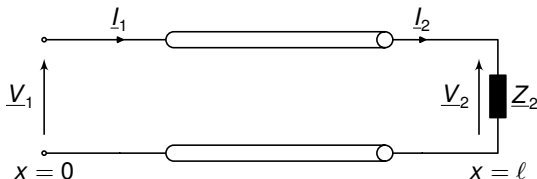
## 2.2 SIL of lossy power line - Sending end (2)




- From solution of wave equation with  $x = 0$  and  $\underline{\gamma} = \alpha + j\beta$  (see EEN320, transmission line characteristics)

$$\begin{aligned} \underline{V}_1 &= \cosh(\underline{\gamma}l)\underline{V}_2 + \underline{Z}_W \sinh(\underline{\gamma}l)I_2 \\ &= \cosh(\underline{\gamma}l)\underline{V}_2 + \underline{Z}_W \sinh(\underline{\gamma}l)\frac{\underline{V}_2}{\underline{Z}_W} \\ &= \underline{V}_2 (\cosh(\underline{\gamma}l) + \sinh(\underline{\gamma}l)) = \underline{V}_2 e^{\underline{\gamma}l} \\ \underline{I}_1 &= \frac{\underline{V}_2}{\underline{Z}_W} \sinh(\underline{\gamma}l) + \cosh(\underline{\gamma}l)I_2 \\ &= I_2 (\cosh(\underline{\gamma}l) + \sinh(\underline{\gamma}l)) = I_2 e^{\underline{\gamma}l} \end{aligned}$$

*at  $j\beta$   
angles  
 $e^{\alpha + j\beta l}$*

Note: To obtain the last equality, we have used  $\cosh(x) + \sinh(x) = e^x$
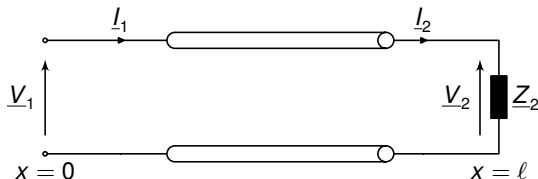
## 2.2 SIL of lossy power line - Sending end (3)



- Apparent power at sending end

$$\underline{S}_1 = P_1 + jQ_1 = \underline{V}_1 \underline{I}_1^* = \underline{V}_2 \frac{\underline{V}_2^*}{\underline{Z}_w^*} e^{2\alpha l} = \underline{S}_2 e^{2\alpha l}$$

$$\frac{S_1}{S_2} = e^{2\alpha l}$$

- As in lossless case, phase angle between voltage and current remains constant along line; phase shift is proportional to  $\beta x$
- But now, active and reactive power decrease with line length; same applies to voltage and current

**Table:** Typical values for OHLs<sup>1</sup>

Rated voltage in kV	132	275	400
$\underline{Z}_w$ [ $\Omega$ ]	373	302	296
$P_{SIL}$ [MW]	47	250	540

**Table:** Typical values for cables<sup>2</sup>

Rated voltage in kV	115	230	500
$\underline{Z}_w$ [ $\Omega$ ]	36.2	37.1	50.4
$P_{SIL}$ [MW]	365	1426	4960


<sup>1</sup> Source: B. M. Weedy et al., "Electric Power Systems", John Wiley & Sons, 2012

<sup>2</sup> Source: P. Kundur, "Power System Stability", McGraw-Hill, 1994


- 1 Decoupled quantities
- 2 Surge impedance loading
- 3 The two extrema: No load and short circuit conditions**
  - No load conditions
  - Short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power (P-V) characteristic of a high-voltage power line
- 8 Angle-active power (P- $\delta$ ) characteristic of a high-voltage power line

- Next, we analyse the behaviour of a power line in two special cases
  - No load
  - Short circuit
- To simplify our calculations, we restrict ourselves to the lossless case


## 3.1 No load conditions - Setup

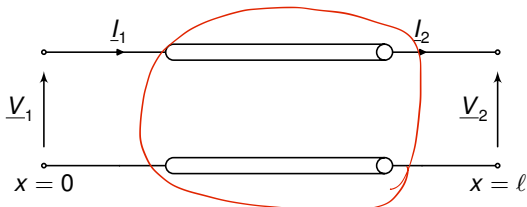

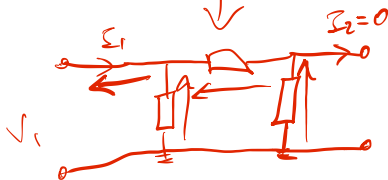- No load condition can occur if
  - Voltage is applied to unloaded line
  - Load at end of line is disconnected
- Main characteristic:  $I_2 = 0$





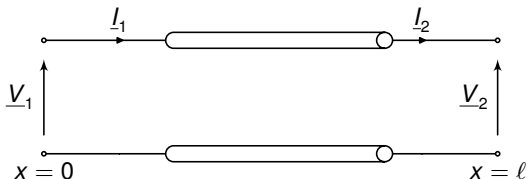

- Solution of wave equation with  $x = 0$  and  $\underline{\gamma} = j\omega\sqrt{L'C'} = j\beta$  yields (see Part 5, Sect. 4.2)


$$\underline{V}_1 = \cos(\beta\ell)\underline{V}_2$$

$$\underline{I}_1 = j\frac{\underline{V}_2}{Z_W} \sin(\beta\ell)$$

- Recall that we may fix one of two voltage angles. Setting  $\varphi_1 = 0$ , we have

$$V_1 = \cos(\beta\ell)V_2$$
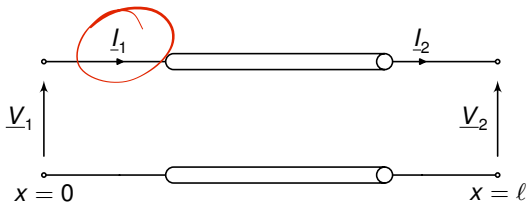
$$I_1 = j\frac{V_2}{Z_W} \sin(\beta\ell)$$






- Keeping  $V_1$  constant, we get

$$V_2 = \frac{V_1}{\cos(\beta\ell)}$$


$$I_1 = \frac{jV_2}{Z_w} \sin(\beta\ell) = \frac{jV_1 \tan(\beta\ell)}{Z_w}$$

- Voltage amplitude increases along line, while that of current decreases ( $I_2 = 0$ )
- This phenomenon is called *Ferranti effect* (because it was first observed by the British engineer Sebastian Ziani de Ferranti in 1887)
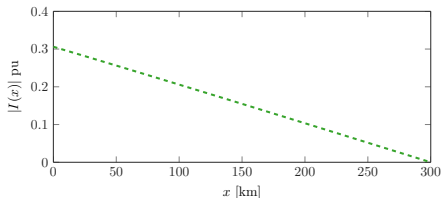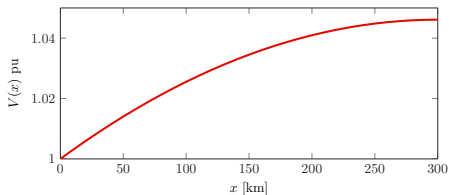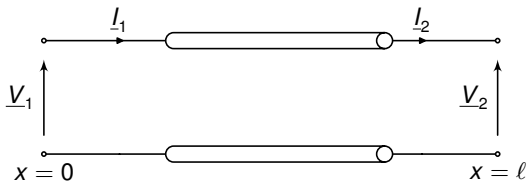
### 3.1 No load conditions - Ferranti effect illustration


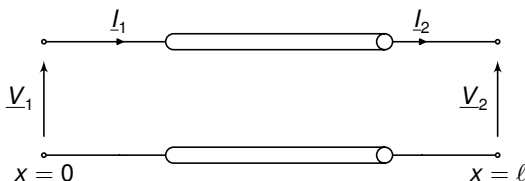
## 3.1 No load conditions - Ferranti effect resonance



- It holds that ( $\epsilon_0$  is electric constant and  $\mu_0$  magnetic constant)


$$\beta = \omega\sqrt{L'C'} \approx \omega\sqrt{\epsilon\epsilon_0\mu_0}$$

- Permittivity of air  $\epsilon = 1$
- For  $\omega = 2\pi 50$  [rad/s], we have that  $\beta \approx \frac{6^\circ}{100 \text{ km}}$

→ Extreme scenario: resonance; achieved for 50 Hz at  $l = 1500 \text{ km}$

$$\beta l = \frac{6^\circ \times 1500 \text{ km}}{100 \text{ km}} = 90^\circ = \frac{\pi}{2}$$

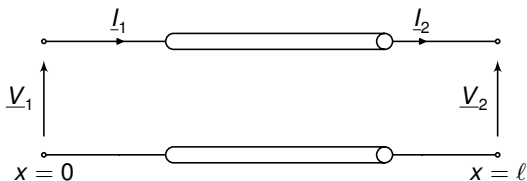- Then  $\cos(\beta l) = 0$  and  $V_2 \rightarrow \infty$




- Impedance at sending end

$$\underline{Z}_1 = \frac{\underline{V}_1}{\underline{I}_1} = -j \frac{Z_w}{\tan(\beta l)}$$

- We can see that impedance has *capacitive* character
- High loading currents required!
- In practice: amplitude of  $\underline{V}_1$  not stiff, but additionally increased by loading currents → need to be careful with voltage rise already for line lengths of 300km
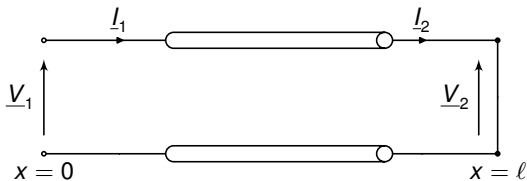
## 3.2 Short circuit conditions - Voltage and current



- Short circuit  $\rightarrow \underline{V}_2 = 0$
- Solution of wave equation with  $x = 0$  and  $\underline{\gamma} = j\omega\sqrt{L'C'} = j\beta$  yields (see EEN320 for more details)


$$\underline{V}_1 = jI_2 Z_w \sin(\beta l)$$

$$I_1 = I_2 \cos(\beta l)$$



- In analogy to voltage in no load condition, now current increases along line

$$I_2 = \frac{I_1}{\cos(\beta l)}$$

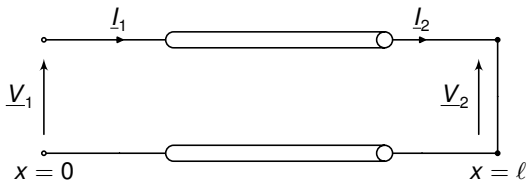


- Short circuit impedance

$$\frac{\underline{V}_1}{\underline{I}_1} = \underline{Z}_1 = jZ_w \tan(\beta l)$$


- For  $\omega = 2\pi 50$  [rad/s], short circuit impedance is *inductive* for line lengths  $< 1500$  km
- As before, resonance  $|\underline{I}_2| \rightarrow \infty$  for  $\beta l = \pi/2$

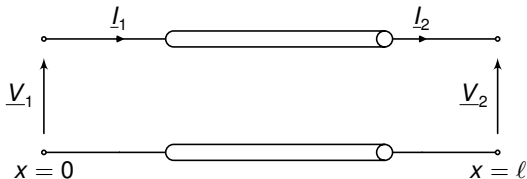- 1 Decoupled quantities
- 2 Surge impedance loading
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line**
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power ( $P-V$ ) characteristic of a high-voltage power line
- 8 Angle-active power ( $P-\delta$ ) characteristic of a high-voltage power line






- Power transmission over a power line causes losses:
  - Ohmic components of line (resistance; conductance) cause active power losses
  - Reactive components of line (inductance; capacitance) influence reactive power flow
- Apparent power at receiving end of line differs from apparent power at sending end!
- For voltage relation along line, reactive power is most important as discussed hereafter for *lossless* line

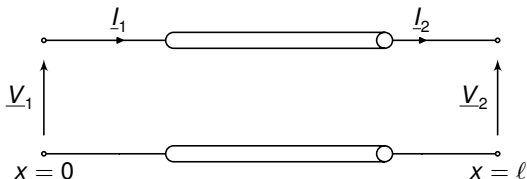

- Wave equation for *lossless* line

$$\begin{bmatrix} \underline{V}_1 \\ \underline{I}_1 \end{bmatrix} = \begin{bmatrix} \cos(\beta l) & jZ_w \sin(\beta l) \\ j\frac{\sin(\beta l)}{Z_w} & \cos(\beta l) \end{bmatrix} \begin{bmatrix} \underline{V}_2 \\ \underline{I}_2 \end{bmatrix}$$

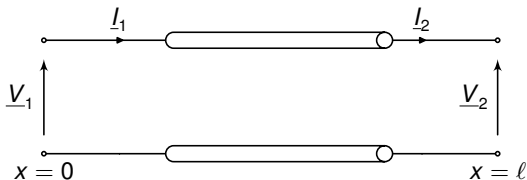→ Apparent power  $\underline{S}_1 = \underline{V}_1 \underline{I}_1^* = P_1 + jQ_1$  at sending end is dependent on  
apparent power  $\underline{S}_2 = \underline{V}_2 \underline{I}_2^* = P_2 + jQ_2$  at receiving end of line



- Hence, we have

$$\underline{S}_1 = \underline{V}_1 \underline{I}_1^* = P_1 + jQ_1 = j \cos(\beta l) \sin(\beta l) \left( |\underline{I}_2|^2 - |\underline{V}_2|^2 \frac{1}{Z_w} \right) + \sin^2(\beta l) \underline{I}_2 \underline{V}_2^* + \cos^2(\beta l) \underline{V}_2 \underline{I}_2^*$$

- For our analysis, it is convenient to fix  $\underline{V}_2$  and express  $\underline{S}_1$  in terms of SIL

$$P_{SIL} = \frac{|\underline{V}_2|^2}{Z_w}$$

- Using the relations

$$|\underline{V}_2|^2 = P_{SIL} Z_w$$

$$\underline{I}_2^* = \frac{\underline{S}_2}{\underline{V}_2} \quad \rightarrow \quad |\underline{I}_2|^2 = \frac{|\underline{S}_2|^2}{|\underline{V}_2|^2} = \frac{|\underline{S}_2|^2}{P_{SIL} Z_w}$$

$$\underline{I}_2 \underline{V}_2^* = (\underline{V}_2 \underline{I}_2^*)^* = \underline{S}_2^* = P_2 - jQ_2$$

$$\cos^2(\beta l) - \sin^2(\beta l) = \cos(2\beta l)$$

$$\cos(\beta l) \sin(\beta l) = \frac{1}{2} \sin(2\beta l)$$

we can rewrite the equation for  $\underline{S}_1$  as follows

$$\underline{S}_1 = P_1 + jQ_1 = P_2 + j \left( Q_2 \cos(2\beta l) + \frac{1}{2} \sin(2\beta l) \left( \frac{|\underline{S}_2|^2}{P_{SIL}} - P_{SIL} \right) \right)$$

- For lossless line

$$P_1 = P_2 \quad \rightarrow \quad \text{can focus further analysis on reactive power flows}$$

- Relation of reactive power flows

$$Q_1 = Q_2 \cos(2\beta\ell) + \frac{1}{2} \sin(2\beta\ell) \left( \frac{|\underline{S}_2|^2}{P_{SIL}} - P_{SIL} \right)$$


- $Q_1$  dependent on  $Q_2$  ("load demand") and reactive power demand of line
- With simplifying approximation  $\cos(2\beta\ell) \approx 1$ , reactive power demand of line given by

$$\Delta Q = Q_1 - Q_2 \approx \underbrace{\frac{1}{2} \sin(2\beta\ell) \frac{|\underline{S}_2|^2}{P_{SIL}}}_{\text{inductive component } Q_L} - \underbrace{\frac{1}{2} \sin(2\beta\ell) P_{SIL}}_{\text{capacitive component } Q_C}$$

- $|\underline{S}_2| = P_{SIL} \rightarrow \Delta Q = 0$
- $|\underline{S}_2| = 0 \rightarrow \Delta Q < 0$  line produces reactive power ( $Q_L = 0, Q_C > 0$ )
- $|\underline{S}_2| > P_{SIL} \rightarrow \Delta Q > 0$  line absorbs reactive power ( $Q_L > Q_C$ )
- $|\underline{S}_2| < P_{SIL} \rightarrow \Delta Q < 0$  line produces reactive power ( $Q_L < Q_C$ )


- 1 Decoupled quantities
- 2 Surge impedance loading
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line**
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power ( $P-V$ ) characteristic of a high-voltage power line
- 8 Angle-active power ( $P-\delta$ ) characteristic of a high-voltage power line
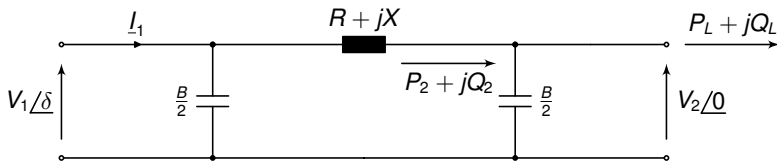
## 5 Voltage drop across a power line - Setup



- $\Pi$ -model of power line of length  $\ell$  and  $G' = 0$ ,  $R = R'\ell$ ,  $X = \omega L'\ell$  and  $B = \omega C'\ell$
- Load at end of line:  $P_L + jQ_L$
- We want to derive a formula for voltage drop across line
- For this purpose it is convenient to define  $V_2$  on real line and denote angle between  $V_2$  and  $\underline{V}_1$  by  $\delta$
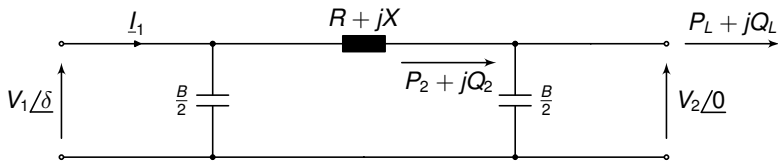
## 5 Voltage drop across a power line - A simplification (1)




- Shunt elements  $B$  produce reactive power
- We can obtain "net" reactive power flow  $Q_2$  on line by subtracting reactive power  $Q_C$  produced by  $B$  from  $Q_L$ , i.e.,

$$P_2 = P_L$$


$$Q_2 = Q_L - Q_C$$


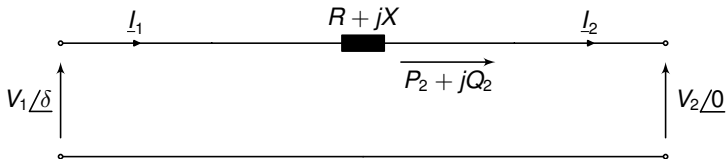
## 5 Voltage drop across a power line - A simplification (2)



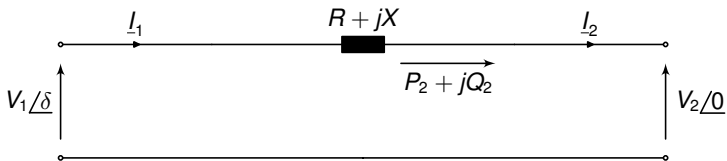- By using  $Q_2 = Q_L - Q_C$  we can simplify considered circuit as shown above



- Current  $I_2$  as function of apparent power  $\underline{S}_2 = P_2 + jQ_2$  and  $\underline{V}_2 = V_2$



$$I_1 = I_2 = \frac{\underline{S}_2^*}{V_2} = \frac{P_2 - jQ_2}{V_2}$$

- Voltage  $\underline{V}_1$


$$\begin{aligned} \underline{V}_1 &= V_2 + (R + jX)I_2 = V_2 + (R + jX)\frac{P_2 - jQ_2}{V_2} \\ &= \left( V_2 + \frac{RP_2 + XQ_2}{V_2} \right) + j \left( \frac{XP_2 - RQ_2}{V_2} \right) \end{aligned}$$

$$|\underline{V}_1| = V_1 = \sqrt{\left( V_2 + \frac{RP_2 + XQ_2}{V_2} \right)^2 + \left( \frac{XP_2 - RQ_2}{V_2} \right)^2}$$
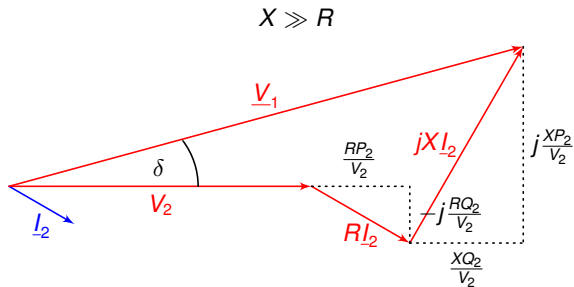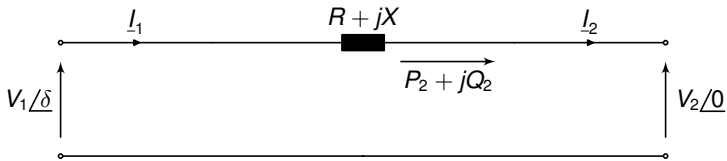
## 5 Voltage drop across a power line - Phasor diagram


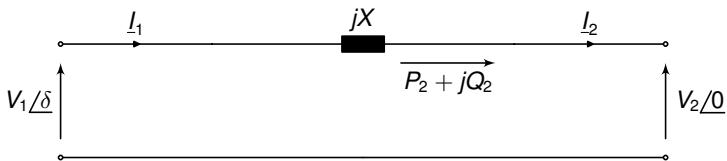
## 5 Voltage drop across a power line - Lossless line




- Lossless line  $\rightarrow R = 0$
- Expression for  $V_1$  simplifies to

$$\underline{V}_1 = V_1 \cos(\delta) + jV_1 \sin(\delta) = \left( V_2 + \frac{XQ_2}{V_2} \right) + j \left( \frac{XP_2}{V_2} \right)$$

- Separating the real with the imaginary parts, gives

$$P_2 = \frac{V_1 V_2 \sin(\delta)}{X}$$
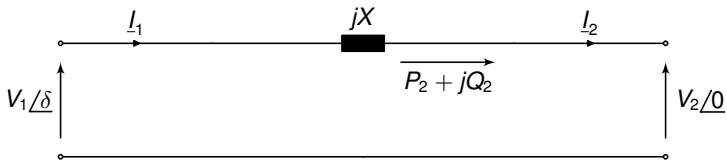
$$Q_2 = \frac{V_1 V_2 \cos(\delta) - V_2^2}{X}$$



- The magnitude of  $V_1$  is given by



$$|\underline{V}_1| = V_1 = \sqrt{\left(V_2 + \frac{XQ_2}{V_2}\right)^2 + \left(\frac{XP_2}{V_2}\right)^2}$$

- In most scenarios  $|XP_2/V_2| \ll V_2$  and expression for  $V_1$  can be further simplified to

$$|\underline{V}_1| = V_1 \approx V_2 + \frac{XQ_2}{V_2}$$


→  $\Delta V = V_1 - V_2$  mainly influenced by reactive power  $Q_2$ !
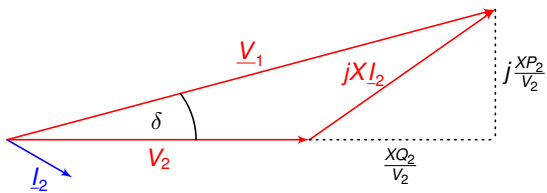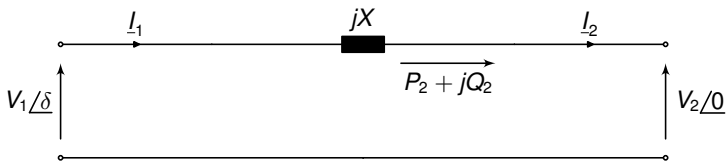
## 5 Voltage drop across a power line - Lossless line phasor diagram



→ Phase angle  $\delta$  mainly influenced by active power  $P_2$ !

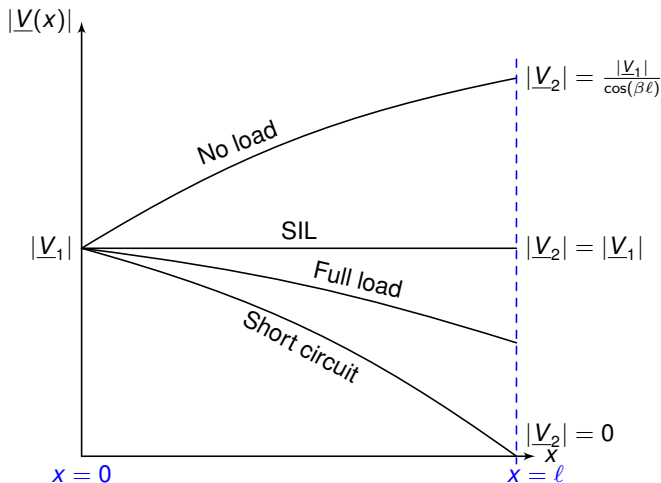
- We have assumed  $V_2$  and  $\underline{S}_2$  are known and we want to calculate  $\underline{V}_1$ ; often also  $V_1$  and  $\underline{S}_2$  given and we seek to compute  $\underline{V}_2$ ; this can be done in an equivalent manner



- The discussed scenarios mainly apply to OHLs; cables typically have different properties

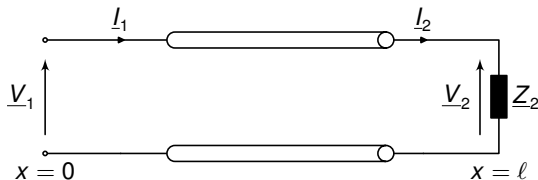- 1 Decoupled quantities
- 2 Surge impedance loading
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line**
- 7 Voltage-active power ( $P-V$ ) characteristic of a high-voltage power line
- 8 Angle-active power ( $P-\delta$ ) characteristic of a high-voltage power line






- Consider exemplary 200 km/420 kV ( $= V_{LL} = \sqrt{3}V_2$ ) power line with following characteristics

$$R' = 0.031 \Omega/\text{km}, L' = 1.06 \text{ mH}/\text{km}, C' = 11.9 \text{ nF}/\text{km}, G' = 0, f = 50 \text{ Hz}$$

- Assume line is loaded with surge impedance  $Z_2 = Z_w$
- Propagation constant

$$\underline{\gamma} = \sqrt{(0.031 + j0.333)j3.74 \cdot 10^{-6}} = (0.052 + j1.117)10^{-3}$$
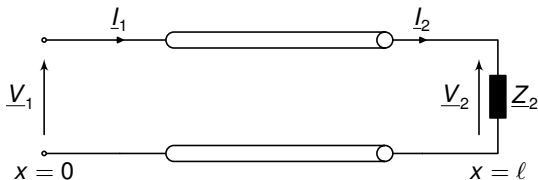
$$\underline{\gamma}l = \alpha l + j\beta l = 0.0104 + j0.2234$$



- Characteristic impedance (neglecting imaginary part)


$$Z_w = 298.5 \Omega$$

- Active power drawn by load at receiving end of line

$$P_2 = \frac{V_{LL}^2}{Z_w} \approx 591 \text{ MW}$$

- Current RMS magnitude (per phase)
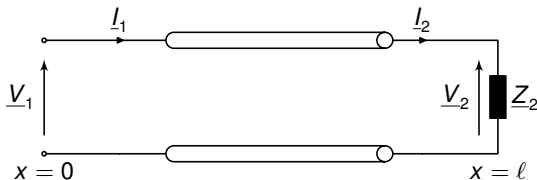
$$I_2 = \frac{\frac{V_{LL}}{\sqrt{3}}}{Z_w} = \frac{420 \text{ kV}}{\sqrt{3} \cdot 298.5 \Omega} = 812.4 \text{ A}$$



- Line losses can be approximated by

$$\Delta P = P_1 - P_2 \approx 3R' l I_2^2 = 3 \cdot 0.031 \cdot 200 \cdot 812.4^2 = 12.3 \text{ MW}$$


- $P_1 = P_2 + \Delta P \approx 591 + 12.3 = 603.3 \text{ MW}$
- Alternative:** We can calculate exact value for  $P_1$  from wave equation (see Part 6 Section 2.2)

$$P_1 = P_2 e^{2\alpha l} = 603.6 \text{ MW}$$


- Our approximation is fairly accurate
- Very high efficiency for power transmission!

$$e^{-2\alpha l} = 0.979 \quad \leftrightarrow \quad 97.9\%$$

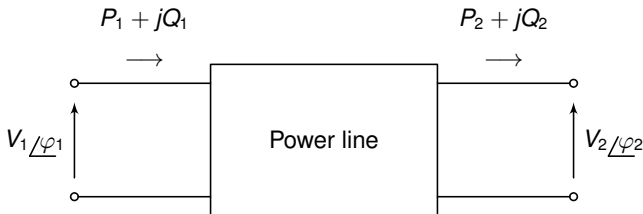- 1 Decoupled quantities
- 2 Surge impedance loading
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power ( $P-V$ ) characteristic of a high-voltage power line**
- 8 Angle-active power ( $P-\delta$ ) characteristic of a high-voltage power line



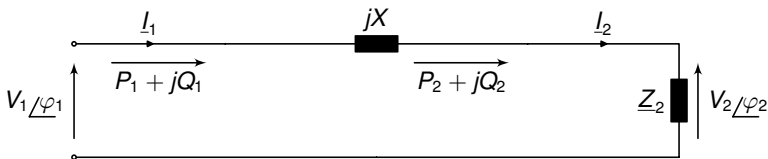- We have seen that power flows over a line affect voltages at sending and receiving end
- If load demand at receiving end is too large, then voltage drop can be significant and even lead to *voltage instability*
- Therefore, it is important to understand relation between voltage drop and load demand




- Suppose that  $V_1 = 1$  pu,  $\varphi_1 = 0$  and that power line is lossless  
 $R' = G' = 0$
- We have that  $I_1 = I_2$ ,

$$\underline{V}_2 = \underline{V}_1 - jX\underline{I}$$

and with  $\delta = \varphi_1 - \varphi_2 = -\varphi_2$

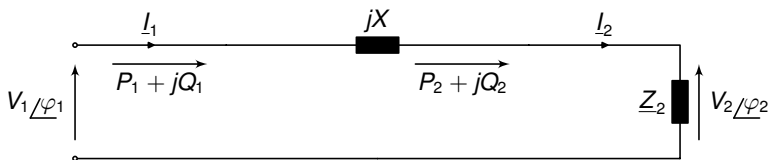
$$\begin{aligned} \underline{S}_2 &= \underline{V}_2 \underline{I}^* = \underline{V}_2 \frac{\underline{V}_1 - \underline{V}_2^*}{-jX} \\ &= \frac{j}{X} \left( V_1 V_2 \cos(\delta) + jV_1 V_2 \sin(\delta) - V_2^2 \right) \end{aligned}$$



- Decomposing  $\underline{S}_2$  in real and imaginary parts yields

$$P_2 = -\frac{V_1 V_2}{X} \sin(\delta)$$
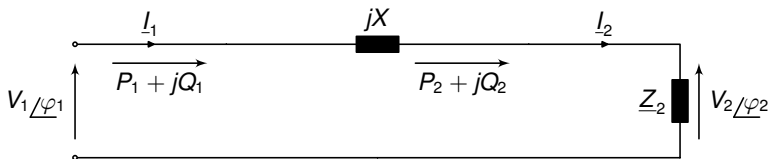
$$Q_2 = \frac{1}{X} \left( V_1 V_2 \cos(\delta) - V_2^2 \right)$$



- Same procedure as for receiving end

$$\underline{S}_1 = \underline{V}_1 \underline{I}^* = \underline{V}_1 \frac{V_1 - V_2^*}{-jX}$$

- Decomposing  $\underline{S}_1$  in real and imaginary parts yields

$$P_1 = \frac{V_1 V_2}{X} \sin(\delta)$$

$$Q_1 = \frac{1}{X} (V_1^2 - V_1 V_2 \cos(\delta))$$

- These equations are called *power flow* or *load flow* equations of the lossless system



- When does a solution to power flow equations exist?

$$\begin{aligned}
 X^2 P_2^2 &= (V_1 V_2 \sin(\delta))^2 \\
 (XQ_2 + V_2^2)^2 &= (V_1 V_2 \cos(\delta))^2 \\
 \Rightarrow 0 &= (V_2^2)^2 + (2Q_2 X - V_1^2) V_2^2 + X^2 (P_2^2 + Q_2^2)
 \end{aligned}$$

- The above is a quadratic equation in  $y = V_2^2$ , i.e.,

$$cy^2 + by + a = 0 \quad c = 1 \quad b = (2Q_2 X - V_1^2) \quad a = X^2 (P_2^2 + Q_2^2)$$

- Condition for existence of at least one real solution (see quadratic formula)

$$\begin{aligned}
 b^2 - 4ac &\geq 0 \\
 \Leftrightarrow (2Q_2 X - V_1^2)^2 - 4X^2 (P_2^2 + Q_2^2) &= V_1^4 - 4X^2 P_2^2 - 4Q_2 X V_1^2 \geq 0
 \end{aligned}$$

- Solution to quadratic equation


$$y_{1,2} = \frac{V_1^2}{2} - Q_2 X \pm \sqrt{\frac{V_1^4}{4} - X^2 P_2^2 - X Q_2 V_1^2}$$

- Voltage magnitude at receiving end

$$V_2 = \sqrt{y_{1,2}} = \sqrt{\frac{V_1^2}{2} - Q_2 X \pm \sqrt{\frac{V_1^4}{4} - X^2 P_2^2 - X Q_2 V_1^2}}$$

- To each loading  $\underline{S}_2 = P_2 + jQ_2$  there exist, in general, two real solutions for  $V_2$ !

## 7 P-V characteristic - $P - V$ curve

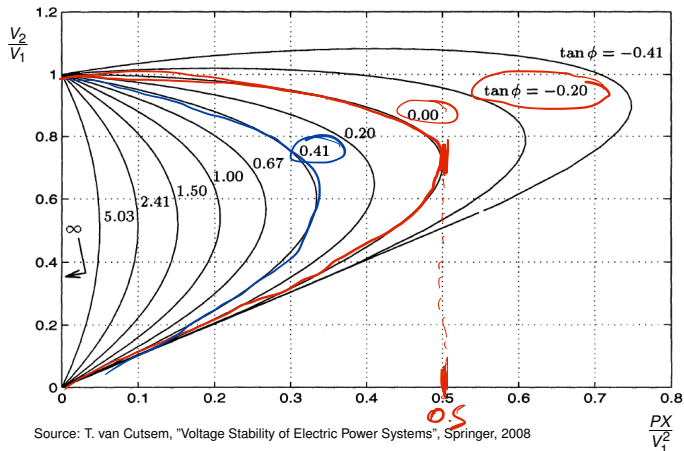

Source: T. van Cutsem, "Voltage Stability of Electric Power Systems", Springer, 2008

$\frac{PX}{V_1^2}$


$$\tan \phi = \frac{Q}{P}$$

- Due to its shape,  $P - V$  curve is also called *nose curve*
- Power factor:  $\cos(\phi) = \frac{P}{|S|} \rightarrow Q = P \tan(\phi)$


- Power transfer is limited by power factor
  - Power factor has significant influence on voltage magnitude at receiving end of line
  - Inductive load ( $\tan(\varphi) > 0$ ): lower transmittible active power and lower voltage magnitude  $V_2$
  - Capacitive load ( $\tan(\varphi) < 0$ ): higher transmittible active power and flatter voltage profile in upper part of nose curve
- Voltage  $V_2$  can be regulated ("parallel compensation") with additional capacitances (compare Part 2 of lecture)
- Specific active power value can be achieved at two different voltage magnitudes
  - Usually, higher value chosen ( $\approx 1$  pu) as results in lower current and also low voltage values can lead to instability

- Power transfer is limited by power factor
  - Power factor has significant influence on voltage magnitude at receiving end of line
  - Inductive load ( $\cos(\varphi)$  ind.): lower transmittible active power and lower voltage magnitude  $V_2$
  - Capacitive load ( $\cos(\varphi)$  cap.): higher transmittible active power and flatter voltage profile in upper part of nose curve
- Voltage  $V_2$  can be regulated ("parallel compensation") with additional capacitances (compare Part 2 of lecture)
- Specific active power value can be achieved at two different voltage magnitudes
  - Usually, higher value chosen ( $\approx 1$  pu) as results in lower current and also low voltage values can lead to instability

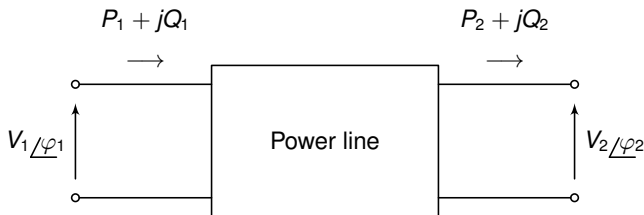- 1 Decoupled quantities
- 2 Surge impedance loading
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power ( $P-V$ ) characteristic of a high-voltage power line
- 8 Angle-active power ( $P-\delta$ ) characteristic of a high-voltage power line**



- Another important relation is that between the transmitted active power flow and the phase angle difference between the voltages at sending and receiving end of line (i.e.,  $\underline{V}_1 = V_1/\underline{\varphi}_1$  and  $\underline{V}_2 = V_2/\underline{\varphi}_2$ )
- We conduct our analysis under the following assumptions
  - The voltage magnitudes  $V_1$  and  $V_2$  are constant
  - The line impedance is purely inductive, i.e.,  $\underline{Z}_\ell = jX = j\omega L'\ell$
- However, the phase angle difference  $\delta = \varphi_1 - \varphi_2$  may vary

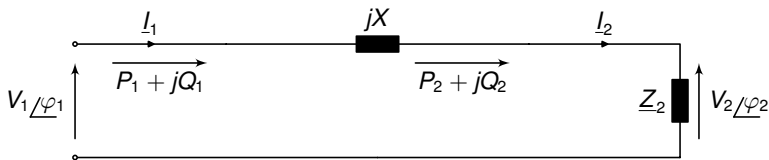

- Voltages in polar form


$$\underline{V}_1 = V_1 e^{j\varphi_1} \quad \underline{V}_2 = V_2 e^{j\varphi_2}$$

- Lossless line  $\rightarrow P_1 = P_2 = \Re(\underline{V}_1 \underline{I}_1^*)$

$$\underline{I}_1 = \underline{I}_2 = \frac{\underline{V}_1 - \underline{V}_2}{jX} = \frac{V_1 e^{j\varphi_1} - V_2 e^{j\varphi_2}}{jX}$$
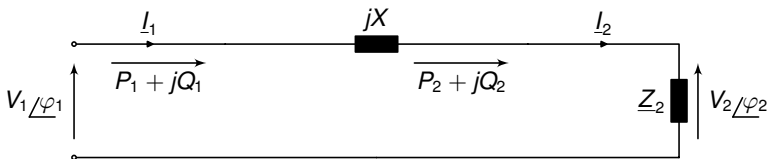
$$\underline{I}_1^* = \frac{V_1 e^{-j\varphi_1} - V_2 e^{-j\varphi_2}}{-jX}$$






- Without loss of generality, we set  $\varphi_2 = 0$
- Then with *transmission angle*  $\delta = \varphi_1 - \varphi_2$

$$\begin{aligned}
 P = P_1 = P_2 &= \Re \left( V_1 e^{j\varphi_1} \frac{j}{X} \left( V_1 e^{-j\varphi_1} - V_2 \right) \right) = \Re \left( jV_1^2 \frac{1}{X} - j\frac{1}{X} V_1 V_2 e^{j\varphi_1} \right) \\
 &= \Re \left( jV_1^2 \frac{1}{X} - jV_1 V_2 \frac{1}{X} \cos(\varphi_1) + V_1 V_2 \frac{1}{X} \sin(\varphi_1) \right) \\
 &= V_1 V_2 \frac{1}{X} \sin(\varphi_1) = V_1 V_2 \frac{1}{X} \sin(\delta)
 \end{aligned}$$
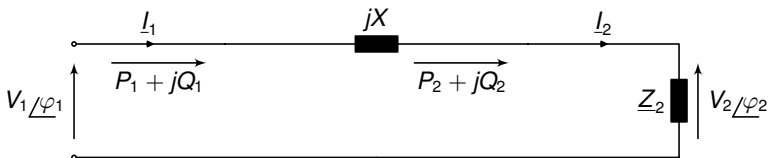
## 8 P- $\delta$ characteristic - Active power flow (2)




- We can rewrite active power in terms of characteristic impedance  $Z_w$ , phase constant  $\beta$  and line length  $\ell$  (see Part 5 Section 4.4)

$$P = P_1 = P_2 = V_1 V_2 \frac{1}{X} \sin(\delta) = V_1 V_2 \frac{\sin(\delta)}{Z_w \sin(\beta\ell)} \quad P_{SIL} = \frac{|V_B|^2}{Z_w}$$
$$\rightarrow \frac{P}{P_{SIL}} = v_1 v_2 \frac{\sin(\delta)}{\sin(\beta\ell)}$$

- Example:  $\ell = 400$  km,  $\beta\ell = 0.52$  rad,  $v_1 = v_2 = 1$  pu

$$P_{\max} = \frac{1}{\sin(\beta\ell)} = 2.012 P_{SIL}$$
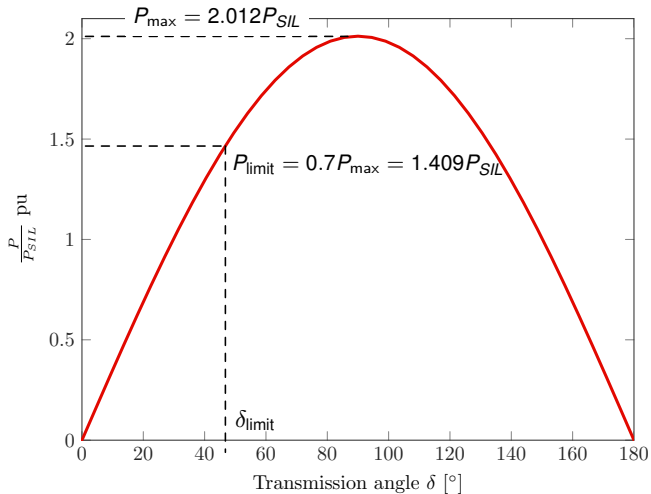
## 8 P- $\delta$ characteristic - Diagram



- $\delta_{\text{limit}} \approx 40^\circ$

- Power lines can not be loaded arbitrarily heavily
- In particular, the following restrictions apply
  - **Thermal limit:** Too high loading can lead to line sag (or rapid ageing in cables)
  - **Voltage drop:** For power quality and stability reasons, voltage magnitude at any bus in a network should not deviate by more than 10% from nominal value
  - **Transmission angle:** For stability reasons, the transmission angle should not exceed a certain maximum value, but a *steady-state stability margin* should be maintained

$$\text{steady-state stability margin} = \frac{P_{\max} - P_{\text{limit}}}{P_{\max}} \cdot 100\% \geq 30\%$$